

High-Speed Digital Operation: Frequency and Delay Requirements

T.C. McDermott, N5EG
Texas Packet Radio Society
June 7, 1996


Outline

- | **Frequency and Group Delay response of optimum Channel**
- | **Partitioning the Response: Modem vs. Radio**
- | **Relationship between Phase and Group delay**
- | **High-pass, Low-pass, All-pass, Band-pass responses**
- | **Equalization**
- | **Some Measured radio responses (with thanks to Bob Morgan, WB5AOH)**


6 Rules for Filter Response

- | **The channel response must be symmetrical around 1/2 the data rate (Nyquist's second theorem, the vestigial symmetry theorem).**
- | **The response should have linear phase.**
- | **The response should cross through the 1/2 amplitude point at one-half the data rate, in baud (Nyquist's first theorem, the minimum bandwidth theorem).**
- | **The spectral shape of the source must be compensated. Generally, we must multiply a square-wave by $x/\sin(x)$.**
- | **The filter transition from passband to stopband should be gentle, not abrupt.**
- | **OPTIONAL:**
- | **To minimize zero-crossing jitter, the impulse response should cross 1/2 amplitude at the one-half bit time.**

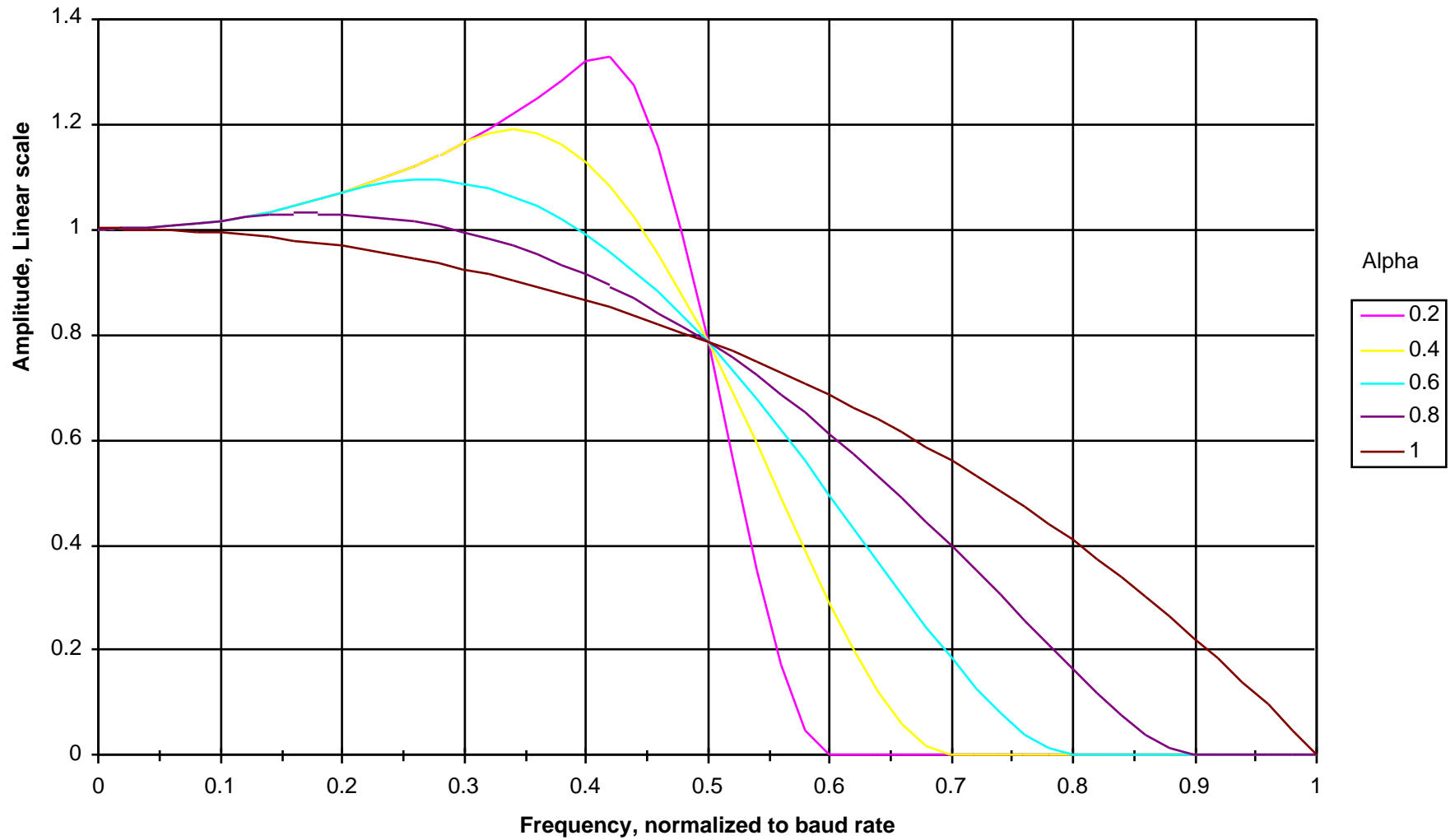Frequency Response of Sinc-compensated Raised-Cosine Filters



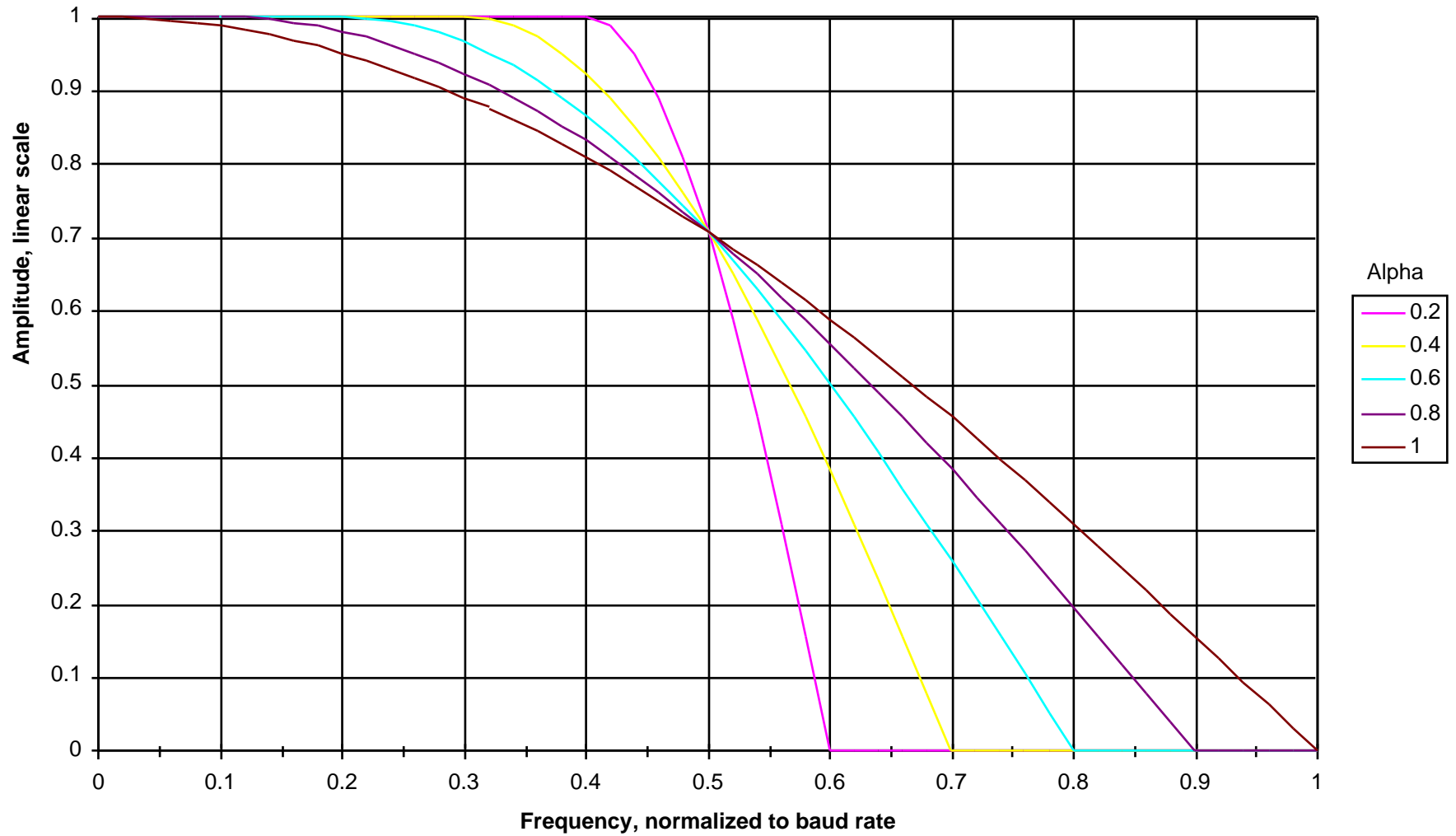Square-root of Raised Cosine Frequency Response



Response Partitioning


- | **Response needs to be well controlled for good performance.**
- | **This is difficult to achieve in the radio - the modem usually contains the precision filters.**
- | **Thus the radio response should be flat in amplitude, and linear in phase**
- | **Linear phase means flat group delay**

Amplitude and Phase of Responses

- | All possible responses can be described as a transfer function using complex numbers**
- | The response consists of Poles and Zeros**
- | Knowing the poles and zeros gives complete knowledge of amplitude, phase and group delay**
- | These can be individually compensated.**


Filters normalized to $RC = 1$ (1 radian/second)

$$s = j 2 \pi f$$

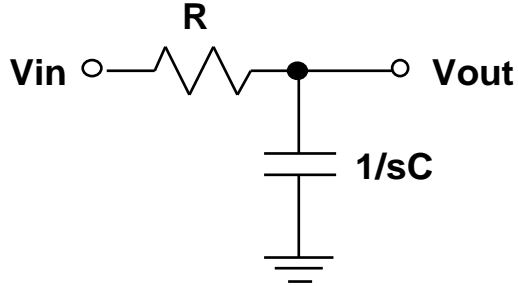


$$V_{out} = \frac{1/sC}{R + 1/sC} = \frac{1}{s+1}$$

Low-pass filter

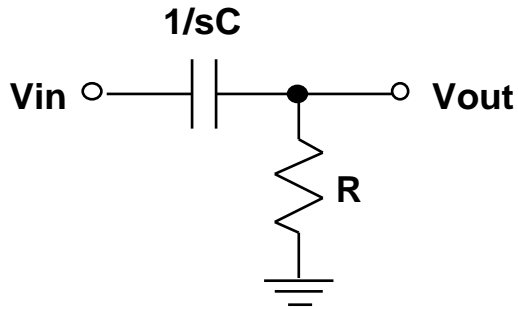

$$V_{out} = \frac{R}{R + 1/sC} = \frac{s}{s+1}$$


High-pass filter

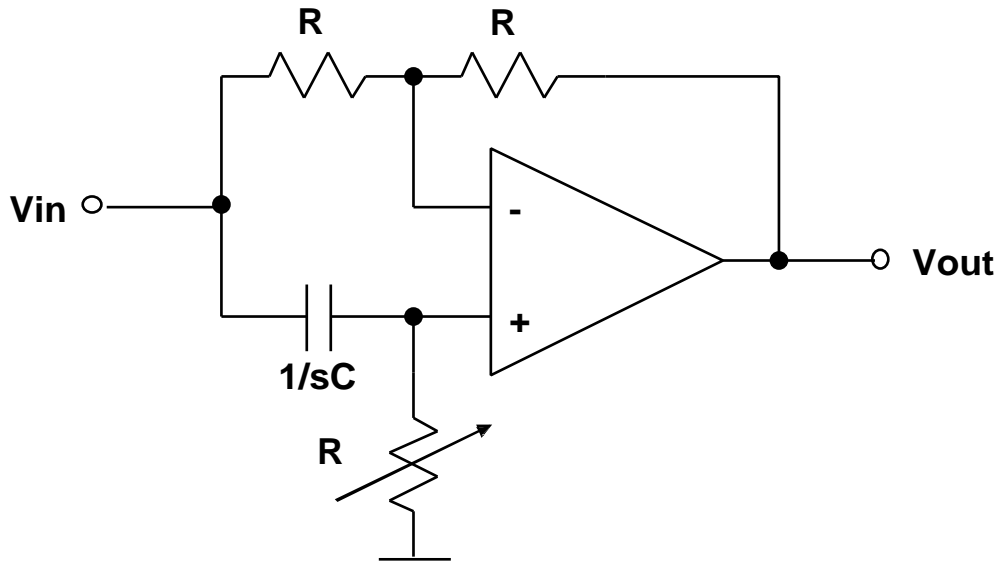


$$V_{out} = \frac{s-1}{s+1}$$

All-pass filter

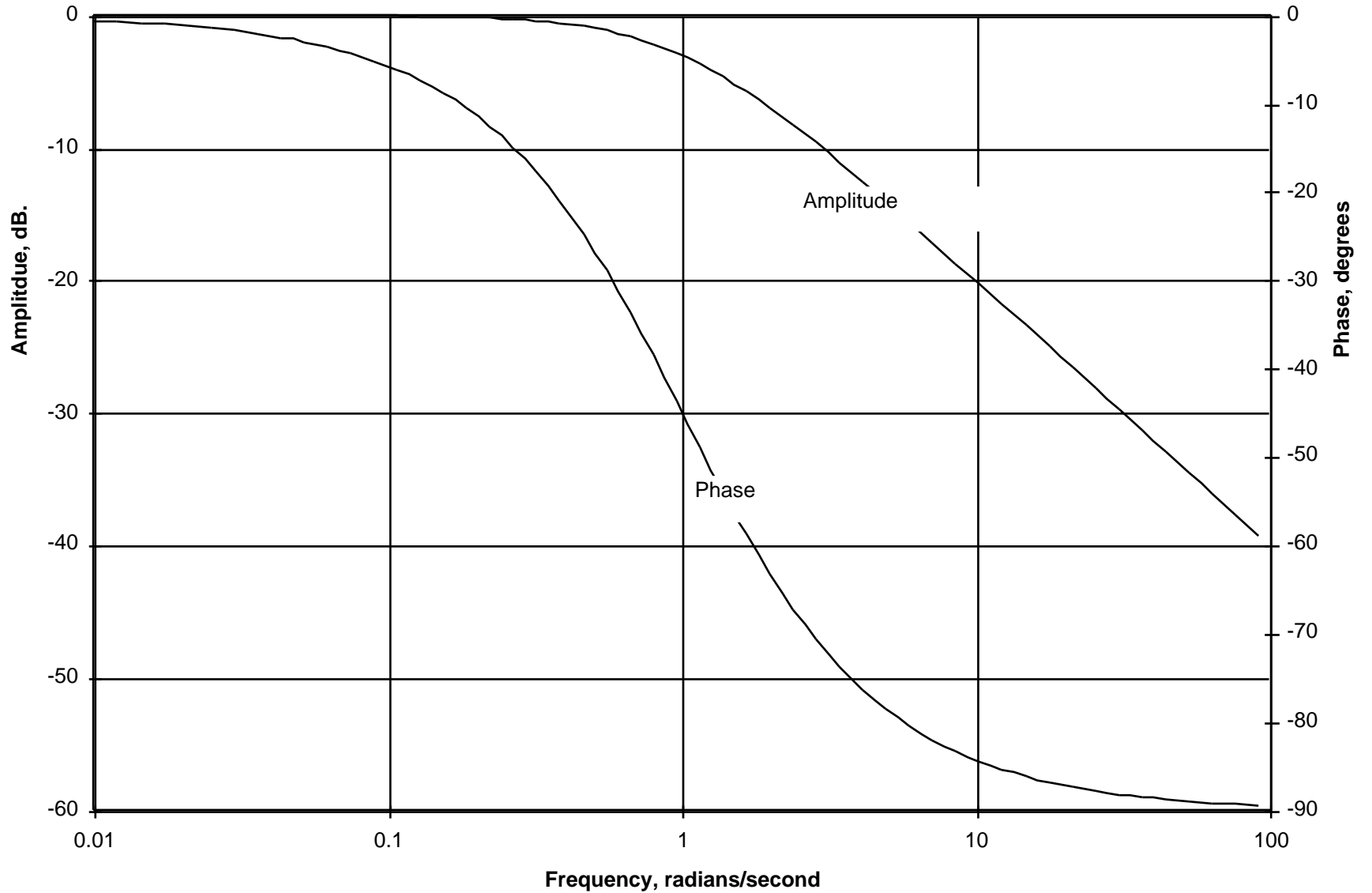Low Pass Filter, normalized to 1 radian/second



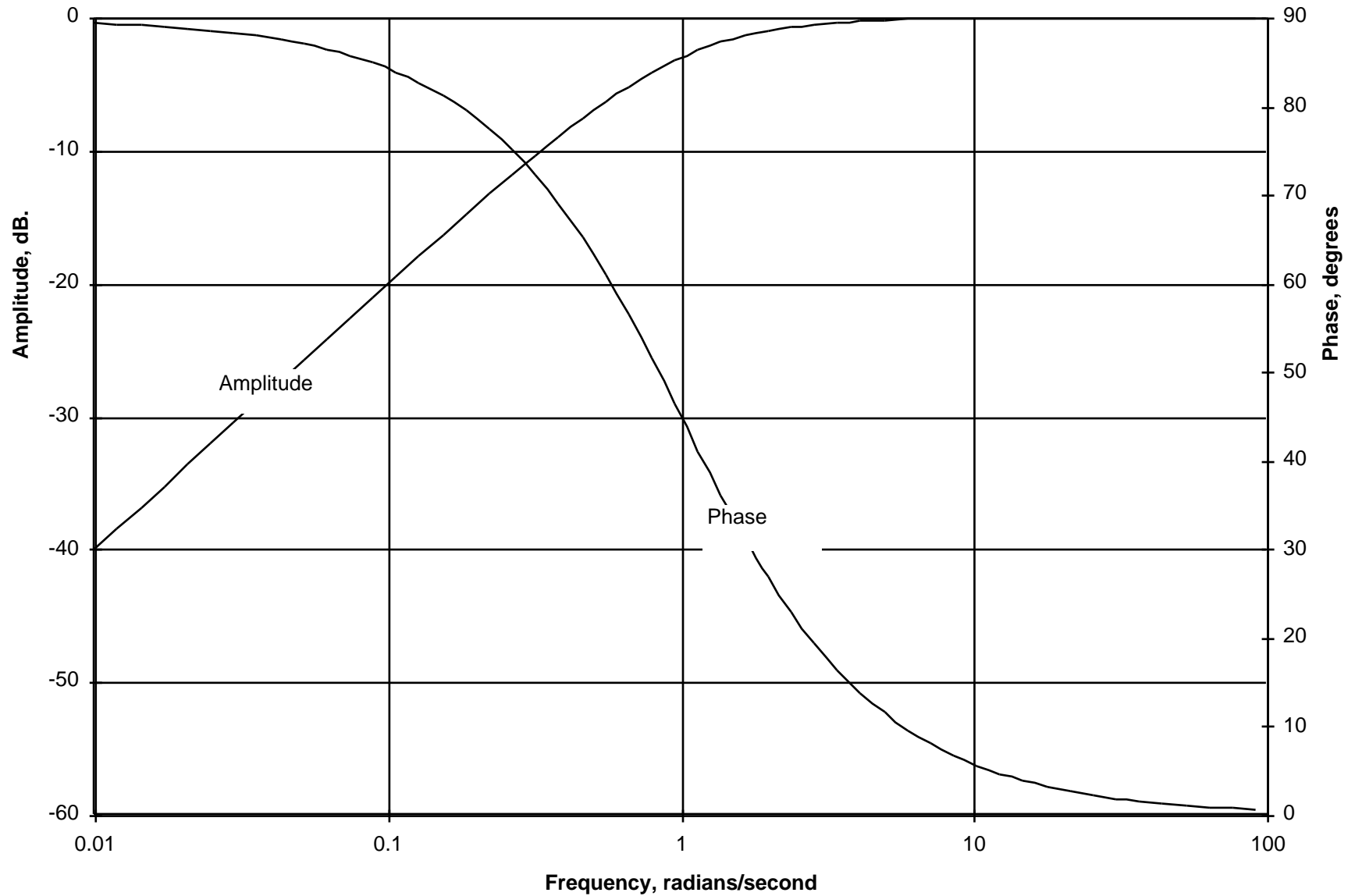High-pass filter, normalized to 1 radian/second



Group Delay

Group delay is the rate of phase-change versus frequency

$$= - \frac{d \text{ phi}}{d \text{ freq}}$$

this is the negative of the 'slope' of the phase versus frequency (negative of the derivative)

Converting units to seconds :


d phi is in radians, d freq is in radians/second. So the units are seconds

$$\text{Radians} = \text{Degrees} * \text{PI} / 180$$


$$\text{Radians / second} = (\text{Cycles / second}) * 2 * \text{PI}$$

$$\text{So, seconds} = (\text{degrees} * \text{PI} / 180) / (\text{cycles/sec} * 2 * \text{PI}) = \text{degrees/hertz} * 1/360$$

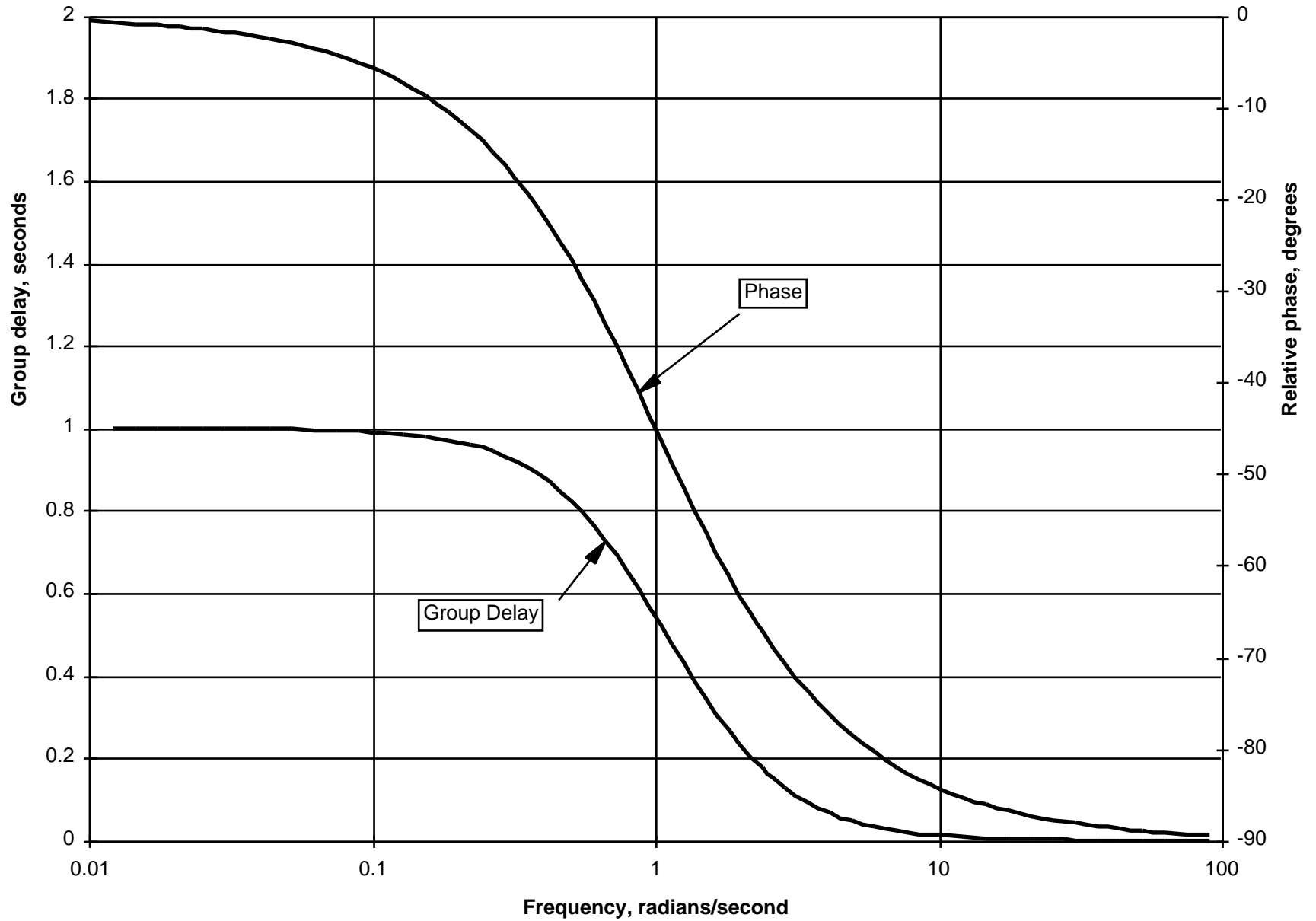
Phase and Group Delay of Low-pass & high-pass filters
normalized to 1 radian/second



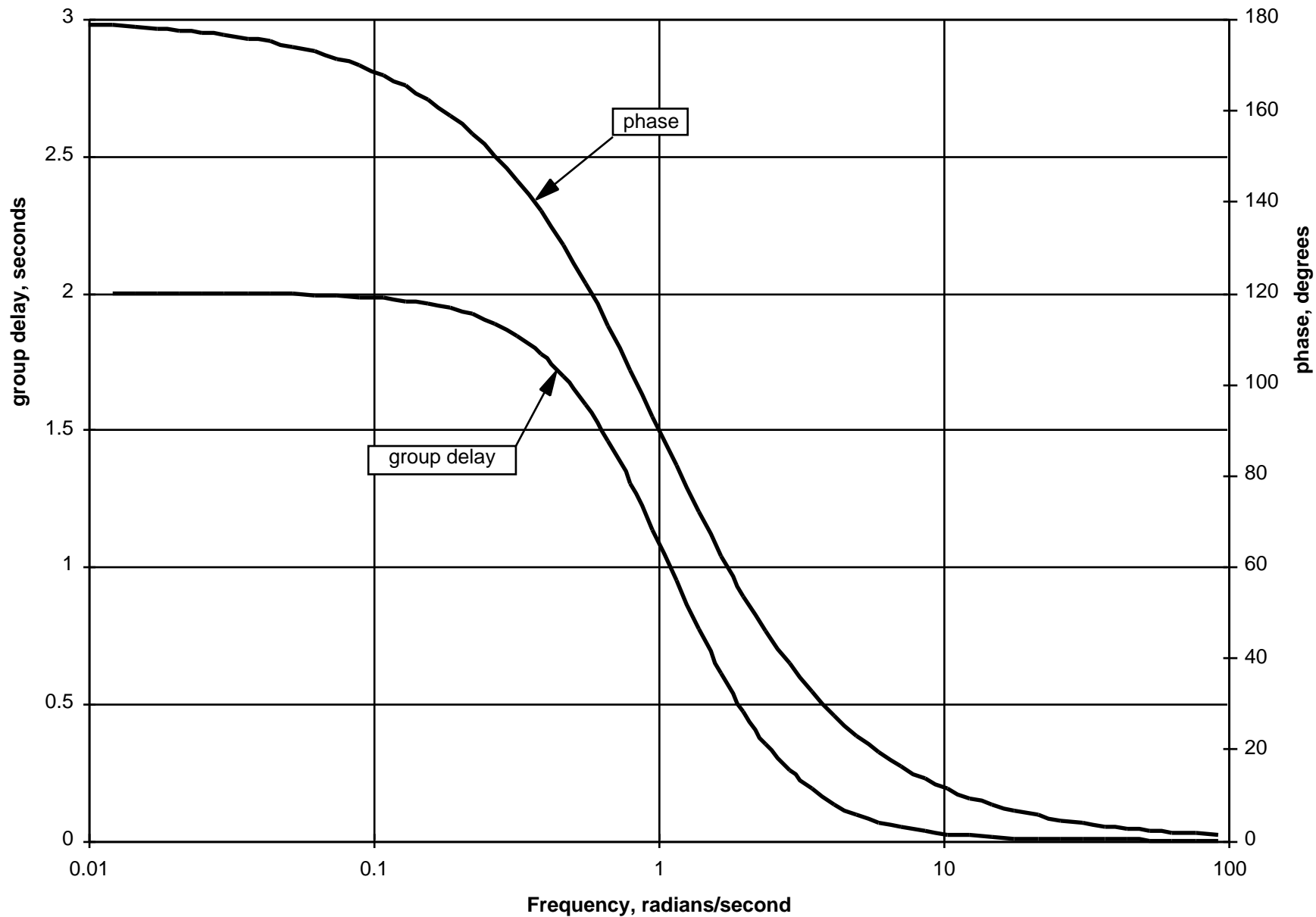
Phase and group delay of equalizer
 $(S-1)/(S+1)$
Normalized to 1 radian/second



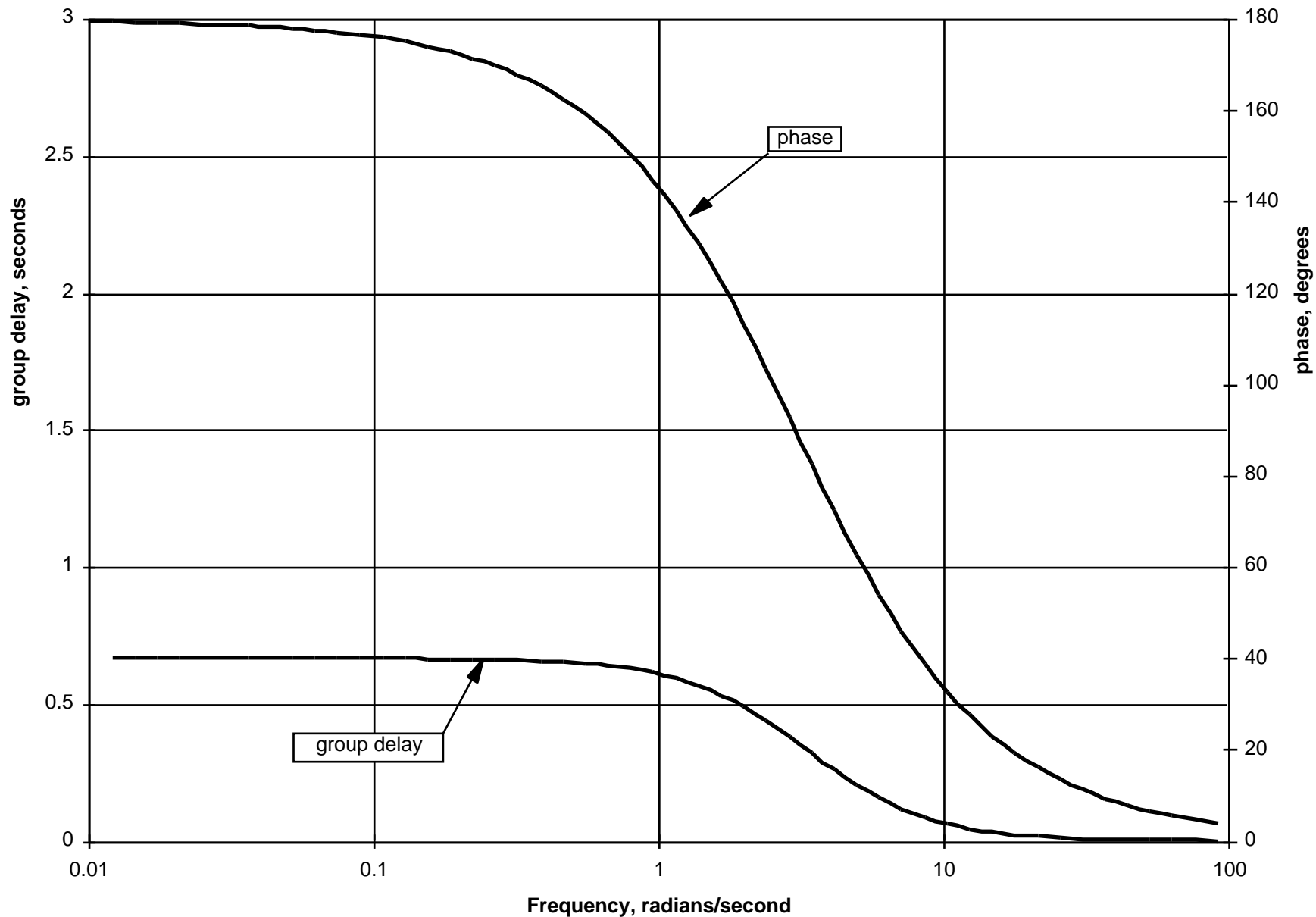
Phase and group delay of equalizer
 $(S-1)/(S+1)$
Normalized to 3 radian/second



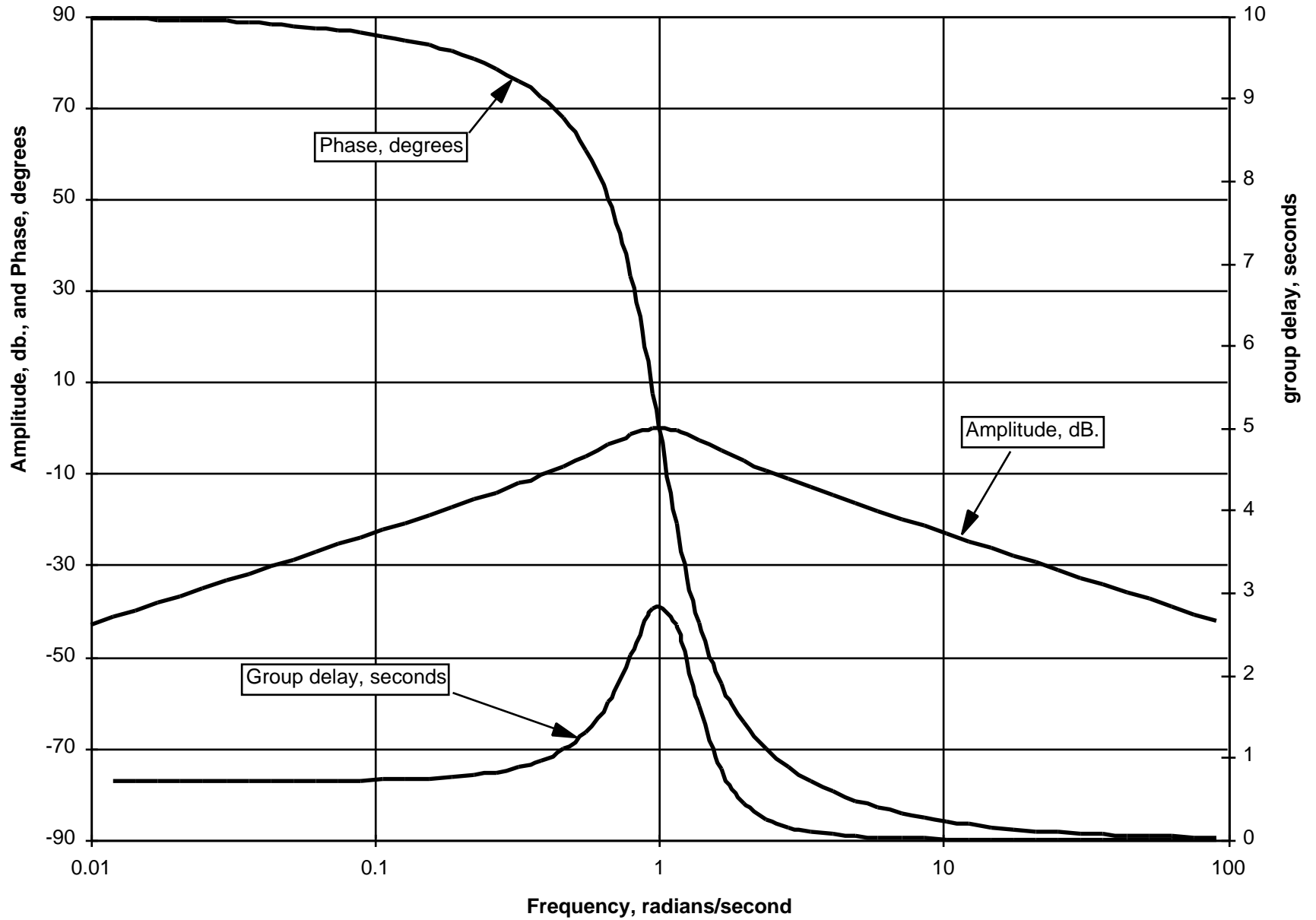
Amplitude, phase, and group delay of RLC bandpass filter
damping = 0.707




6-pole Bandpass Filter

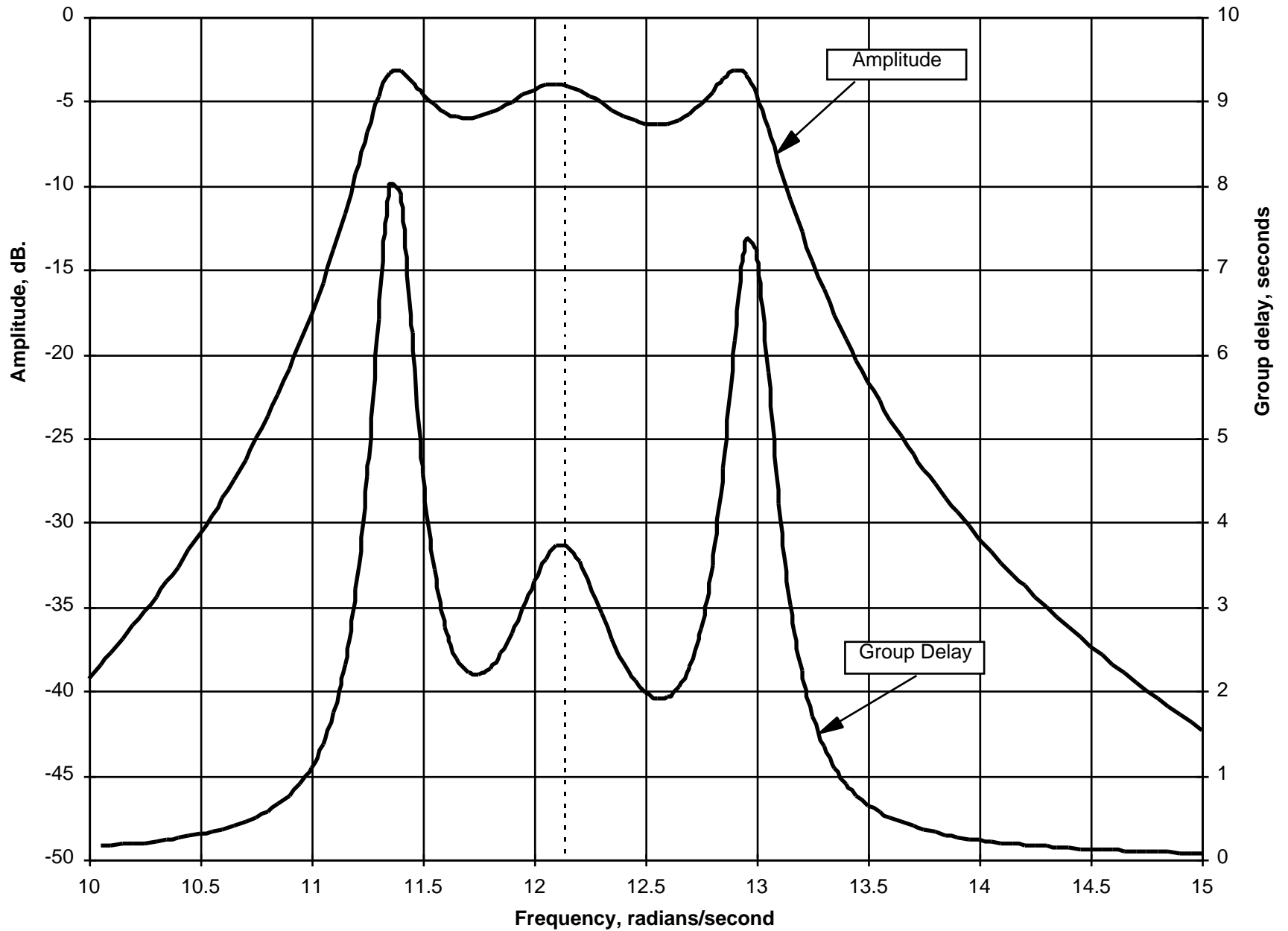


6-pole Butterworth bandpass filter

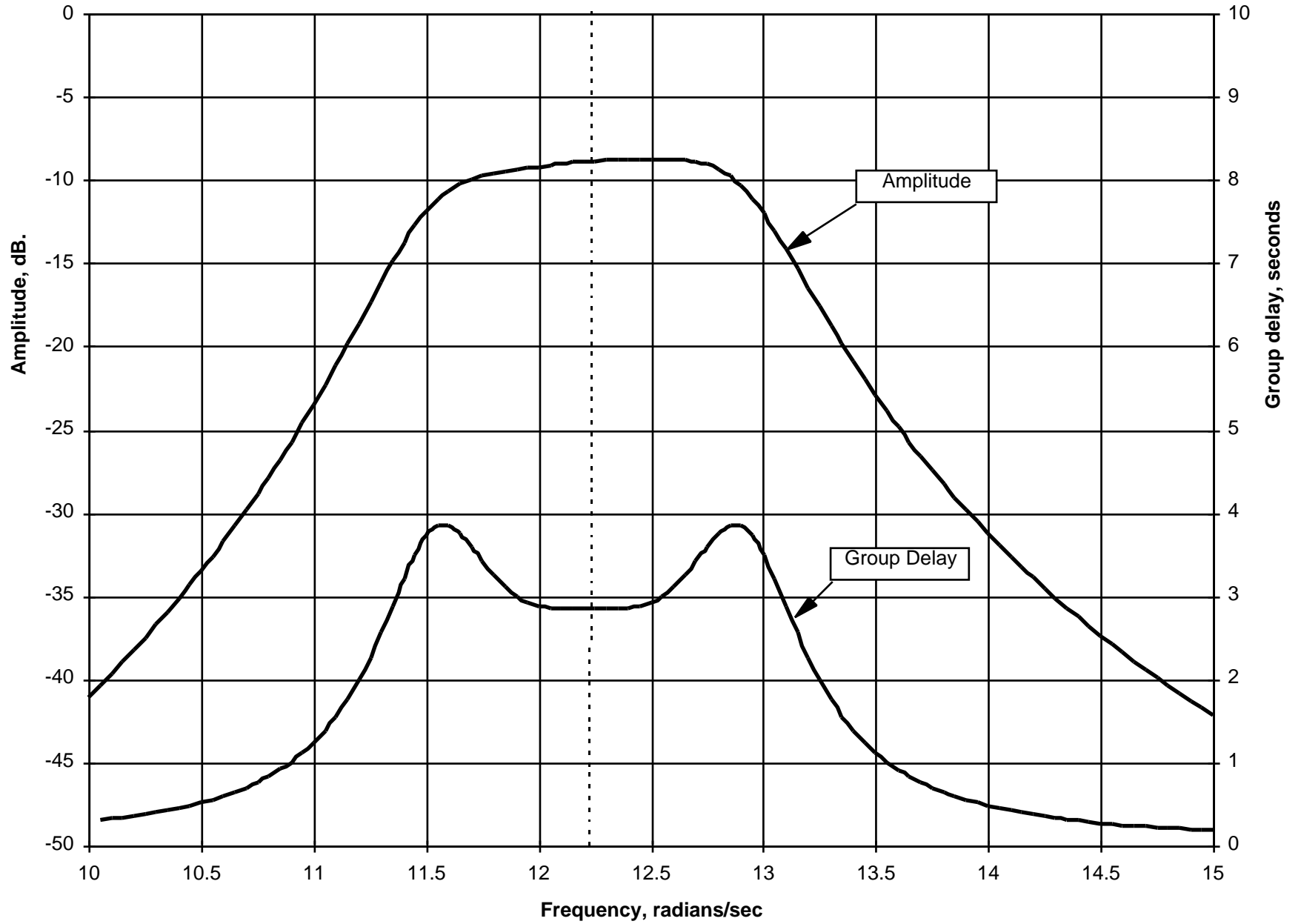


8-pole Chebychev Type-1 filter

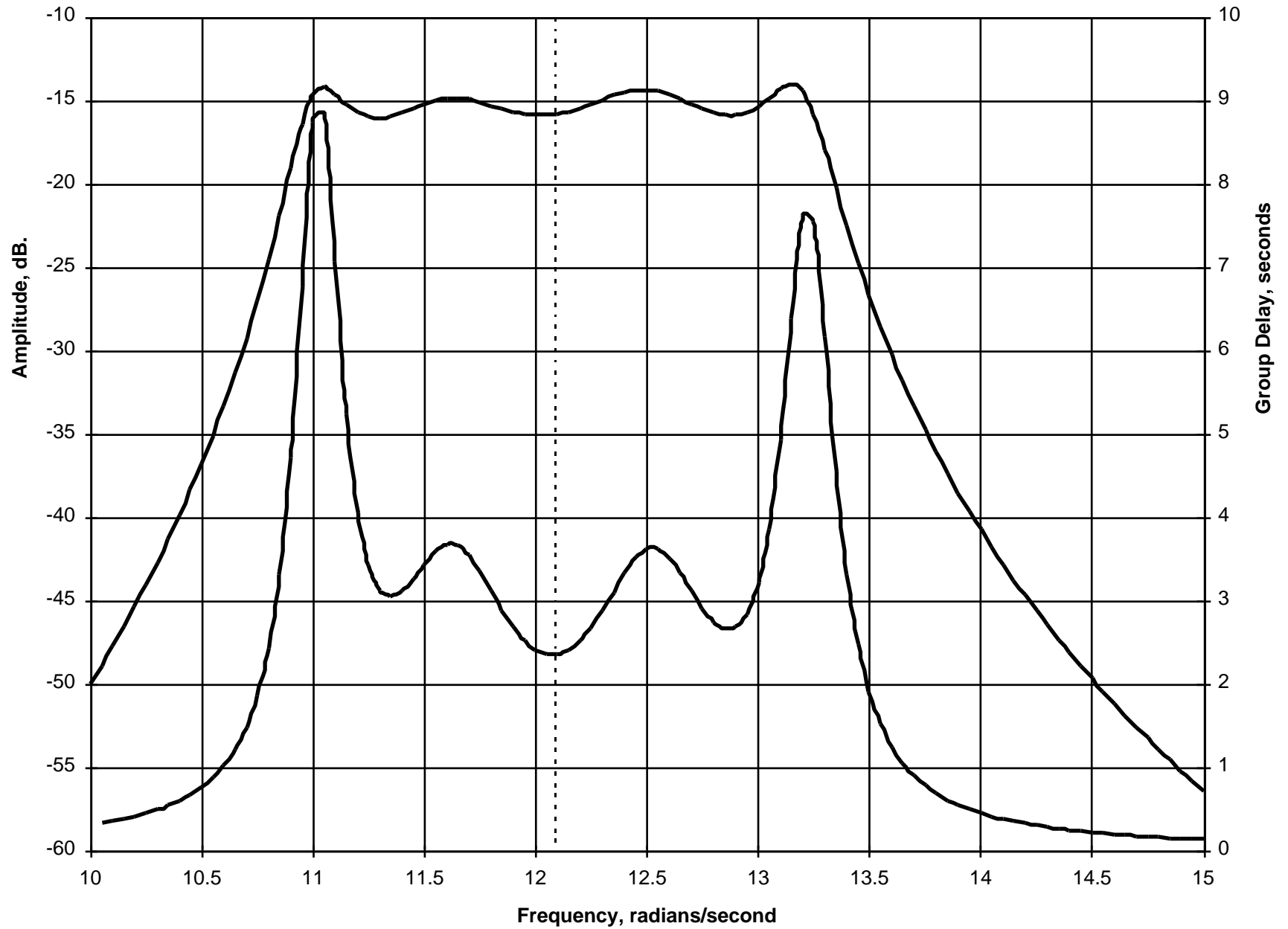


GE Master Exec

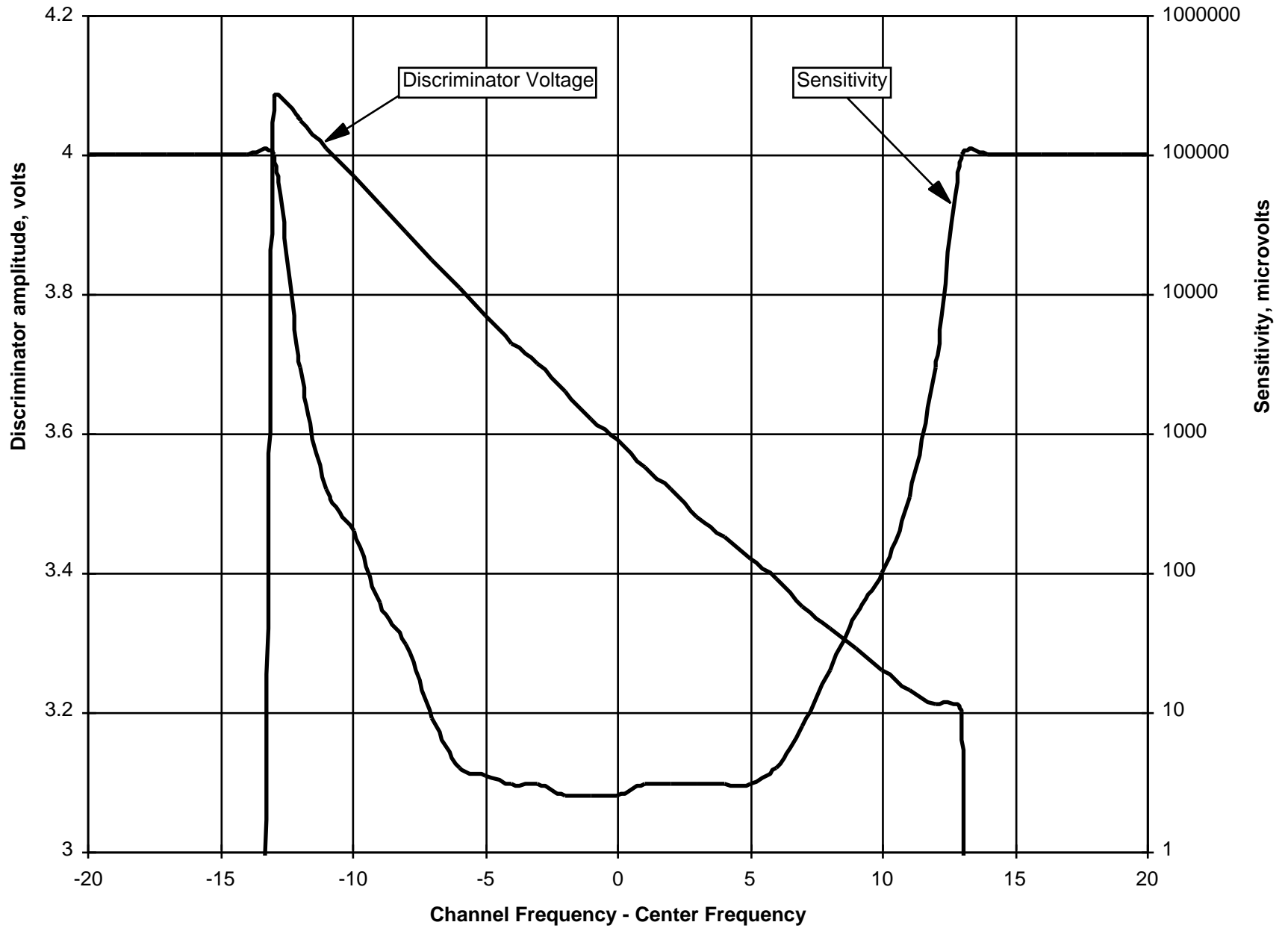

GE Master Exec

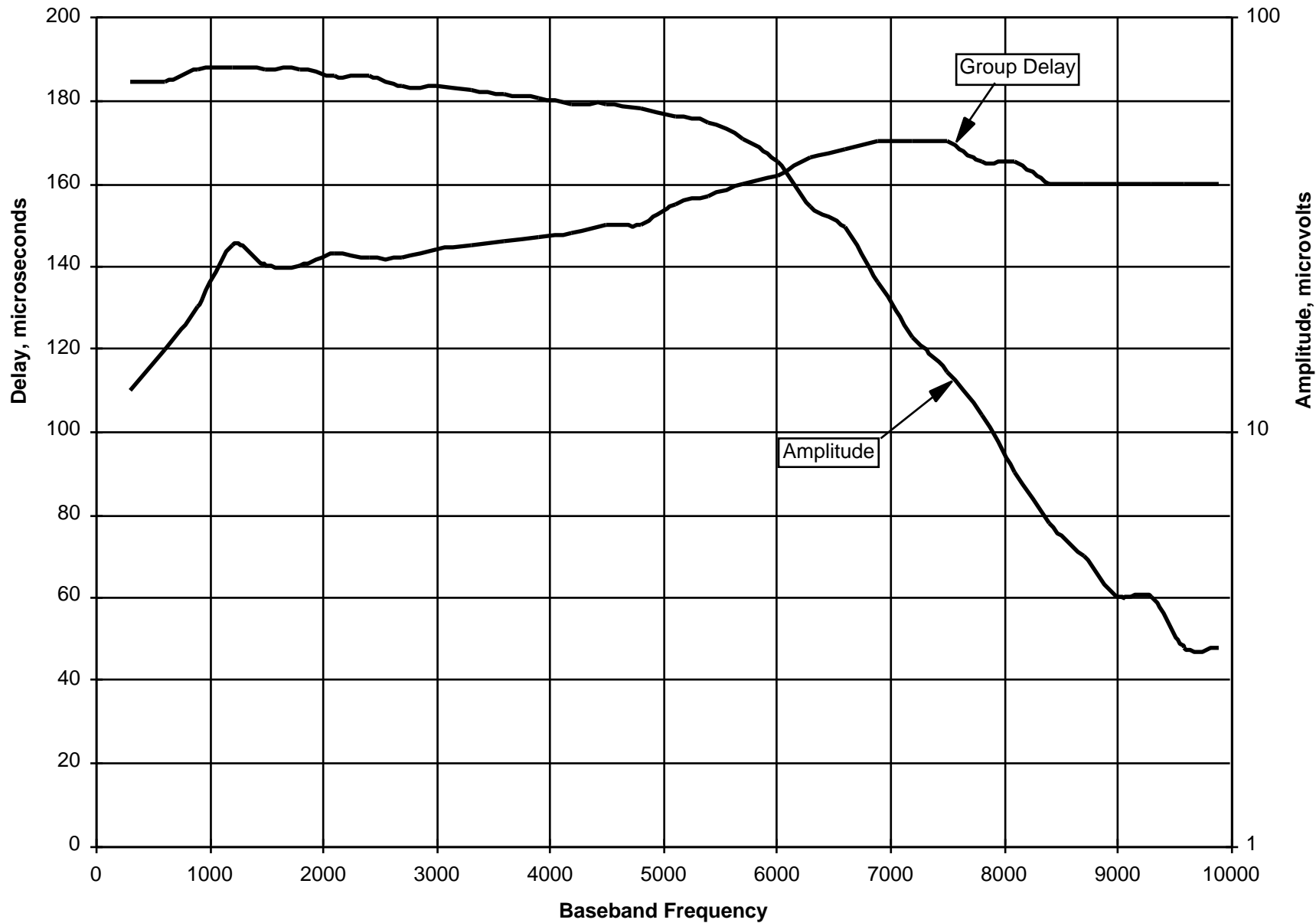

RCA700

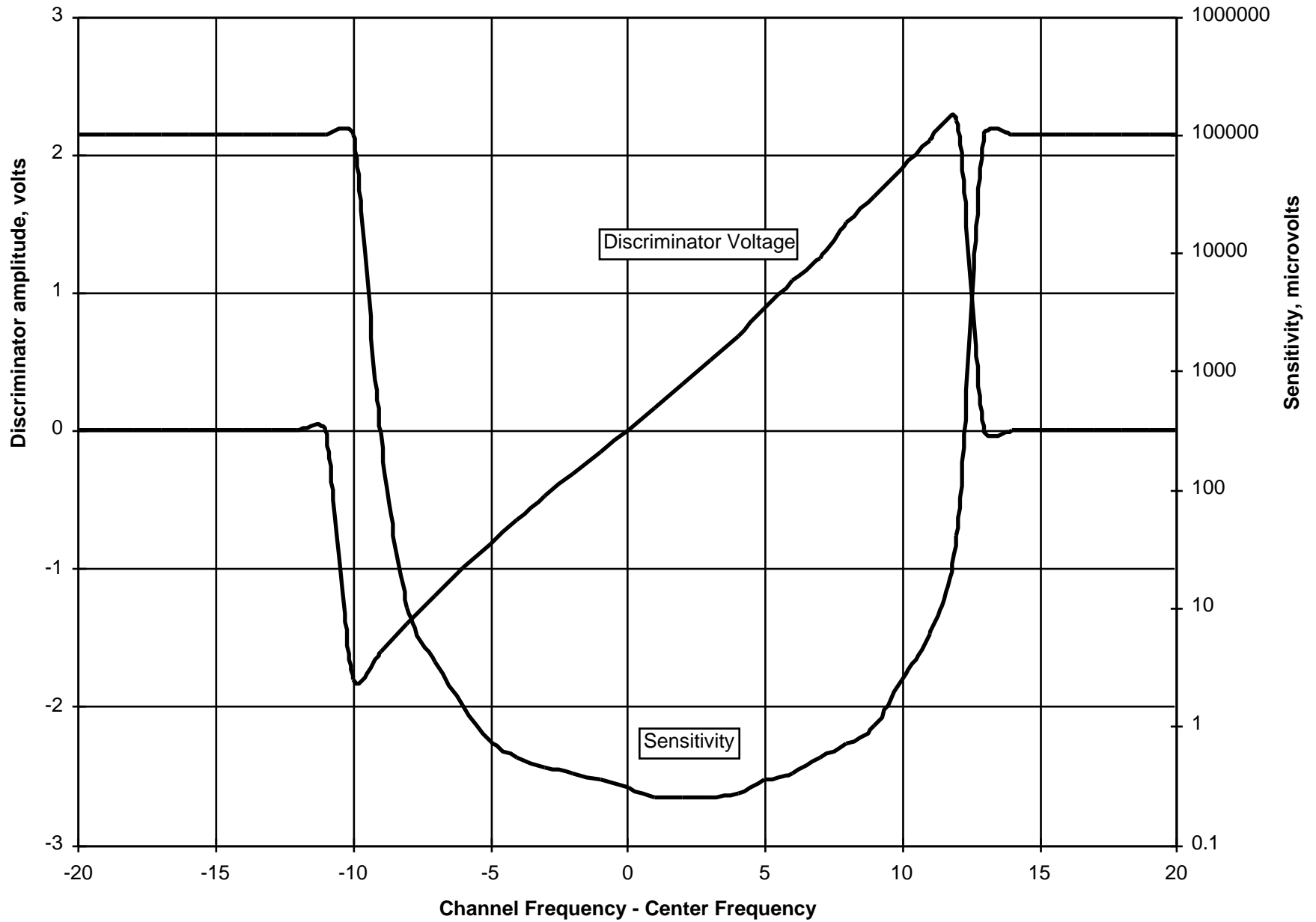

RCA700

